 


Name: Rasha Mansour

ID:1210773

### 5.3 Pre Lab

1) Design the Logic Diagram, function table of the SR latch using NOR gates, and explain how it works.



How It works: SR latches (set/reset) is an asynchronous circuit, the SR latch is a key circuit in digital storage units, when both S and R equals to 0, the output Q remains the same. This is a memory function of the SR latch, it has two inputs, namely set(s) and reset ( r) and two output namely Q and  $\bar{Q}$ . the SR latch operates by storing a bit (either 0 or 1) and then latching onto it until it receives a new input.

-case1: when  $R=0$  and  $S=0$

Suppose initially the value of a Q is 0, then both of the lower Nor gate becomes 0 and the output of the gate become 1 (example  $Q' = 1$  now in the upper gate will be zero and 1 so the output  $Q=0$ , it's called memory condition\ hold state.

-case2: when  $R=1$  and  $S=0$

At the upper Nor gate we will receive output as 0 ,(example  $Q = 1$  now at the lower nor gate we have both inputs 0 , $Q' = 1$  ),it is called rest condition.

-case3: when  $R=0$  and  $S=1$

In this case output at of the second Nor gate will be 0 (example,  $Q' = 0$ ,  $Q = 1$ ), it is called set condition.

-case2: when  $R=1$  and  $S=1$

at both gates, the gate out about Q and  $Q' = 0$ , which is absurd and doesn't follow the basic. It is called invalid state or forbidden state.

